

	Mentor and TA	Mentor and TA	Mentor and TA	Mentor and TA	Mentor and TA
Name	Mr Varma	Mr Dhayal	Ms Skanda	Ms Sameera	Mr Zubair
Experiments	coe16d001@iiitdm.ac.in	edm17d002@iiitdm.ac.in	edm17d001@iiitdm.ac.in	coe18d002@iiitdm.ac.in	coe20d003@iiitdm.ac.in
Exp2	Magic Tool - 3-input AND gate Layout Design Practice - Draw the 3-input AND gate layout, extract the circuit persitics and verify its operation.	Magic Tool - 2-input AND gate Layout Design Practice - Draw the 2-input AND gate layout, extract the circuit persitics and verify its operation.	Magic Tool - 3-input OR gate Layout Design Practice - Draw the 3-input OR gate layout, extract the circuit persitics and verify its operation.	Magic Tool - 3-input NOR gate Layout Design Practice - Draw the 3-input NOR gate layout, extract the circuit persitics and verify its operation.	Magic Tool - 3-input NAND gate Layout Design Practice - Draw the 3-input NAND gate layout, extract the circuit persitics and verify its operation.